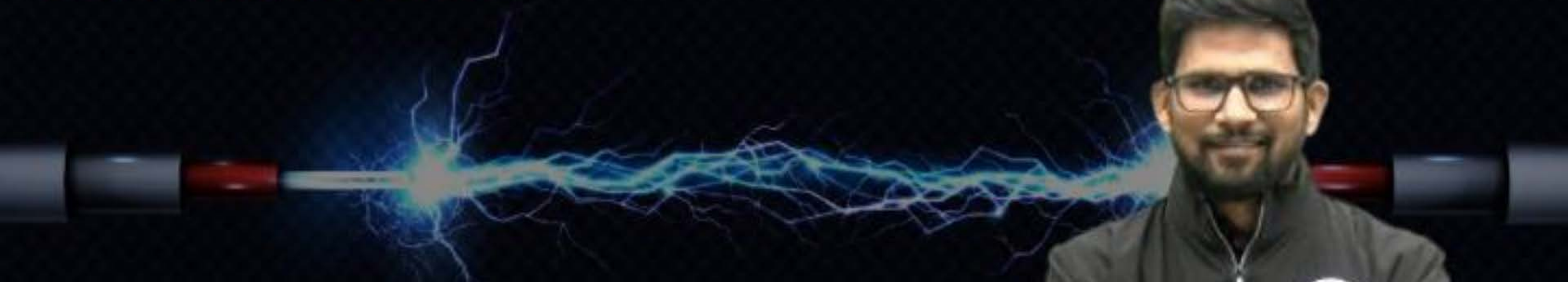


# COMPUTER SCIENCE & IT

## DIGITAL LOGIC



Lecture No. 01

Combinational Circuit



By- Chandan Gupta Sir



# Recap of Previous Lecture

Question Practice





# Topics to be Covered

Comb. CKt.



Q.  $\bar{A}B \oplus \bar{B}C \oplus A\bar{B}C$  is equal to

a.  $\bar{A}B + \bar{A}C$

b.  $\bar{A}B + \bar{B}C$  X

c.  $A\bar{B} + \bar{B}C$  X

d.  $A\bar{B} + \bar{A}C$

P	Q	P.Q
$\bar{A}B$	$\bar{B}C$	$A\bar{B}C$
$\bar{A}B \cdot \bar{B}C = 0$		

$$\bar{A}B \oplus [\bar{B}C \oplus A\bar{B}C]$$

$$\begin{aligned}\bar{A}B \oplus [\bar{B}C(1 \oplus A)] &= \bar{A}B \oplus [\bar{A}\bar{B}C] = \bar{A}B + \bar{A}\bar{B}C = \bar{A}[B + \bar{B}C] \\ &= \bar{A}[(B + \bar{B})(B + C)] \\ &= \bar{A}B + \bar{A}C\end{aligned}$$

$$\bar{A}B \oplus \bar{B}C \oplus A\bar{B}C$$

$$\Sigma(2,3) \quad \Sigma(1,5) \quad \Sigma(5)$$

$$\bar{A}B$$

0	1	0	→ 2
0	1	1	→ 3

$$\bar{B}C$$

0	0	1	→ 1
1	0	1	→ 5

$$A\bar{B}C$$

1	0	1
---	---	---

$$= \Sigma(1,2,3)$$

$$= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC$$

$\uparrow \quad \quad \quad \uparrow$   
 $\bar{A}B$

$$= \bar{A}B + \bar{A}\bar{B}C$$

$$= \bar{A}[B + \bar{B}C]$$

$$= \bar{A}[B + C]$$

$$= \bar{A}B + \bar{A}C$$



•  $f(A, B, C) = \Sigma(3, 5, 6, 7) = \Pi(0, 1, 2, 4)$  self dual

$$\bar{f} = \Sigma(0, 1, 2, 4) = \Pi(3, 5, 6, 7) \longrightarrow \text{self dual}$$

✓✓  
Note:  $\rightarrow$  if  $f$  is self dual boolean function then  $\bar{f}$  will be definitely 'a self dual boolean function.

# [ Type of Digital Circuit ]

- Combinational Circuit
- Sequential Circuit

Comb. CKt.

1. O/p depends on present i/p only.
2. There is no feedback.
3. There is no memory.

• eg. H.A., F.A, H.S., F.S., MUX, decoder, Encoder etc.

Seq. CKt.

1. O/p depends on present i/p and past i/p.
2. There is feedback.
3. There is memory.

eg F.F., Counters, Shift registers  
Johnson Counter etc.

# [ How to Design Combinational Circuit ]




1. Identify the no. of i/p lines & no. of o/p lines ✓

2. Write down the truth table b/w i/p lines and o/p lines.

3. Write down O/Ps in terms of SOP or POS

4. Then simplify every O/P using Boolean theorem or K-Map.

5. Now implement the O/Ps using gates.

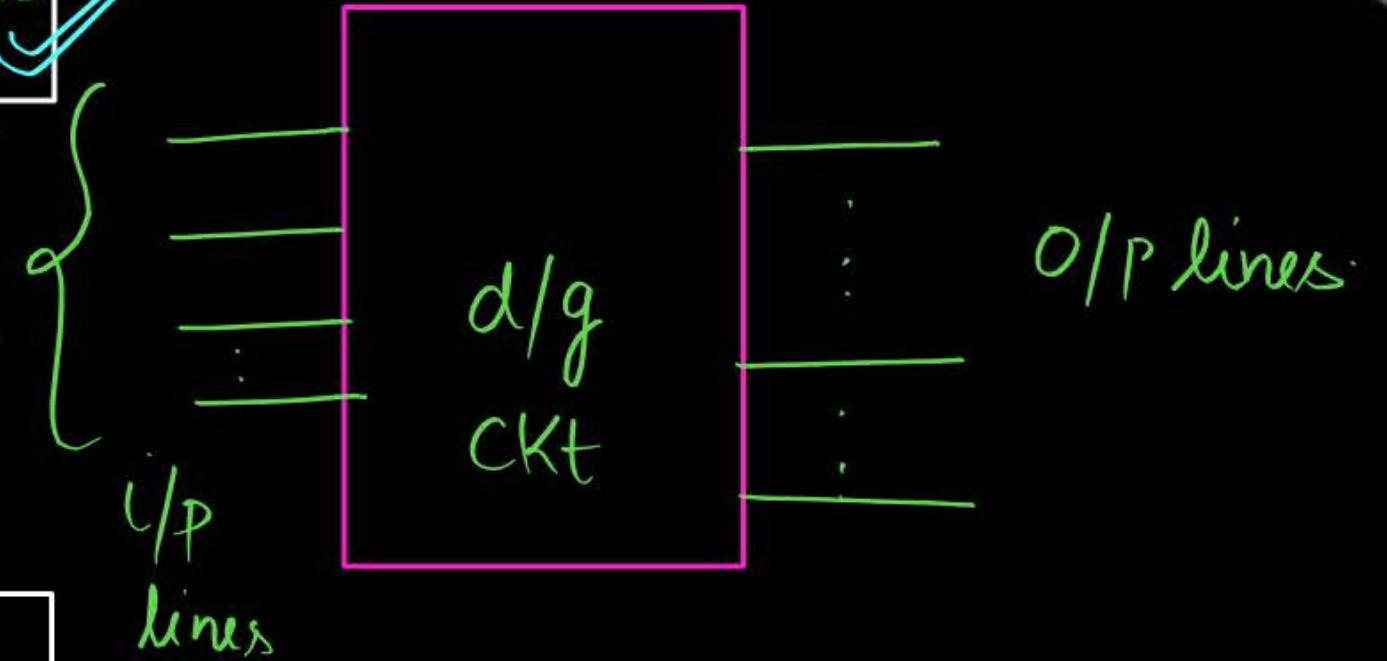



$x$	$y$	$z$	$y_5$	$y_4$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

000  
⋮  
111

$$y_0(x, y, z) = \sum(1, 3, 5, 7) = 3$$



0  
1  
4  
9  
16

$$y_5(x, y, z) = \sum(6, 7)$$

$$y_4(x, y, z) = \sum(4, 5, 7)$$

$$(49) \quad y_3(x, y, z) = \sum(3, 5)$$


$$y_2(x, y, z) = \sum(2, 6)$$

$$y_1(x, y, z) = \sum(\text{nil}) = 0$$

$$y_5 = \Sigma(6,7)$$

$$= \underline{xy\bar{z}} + xyz$$

$$= xy$$

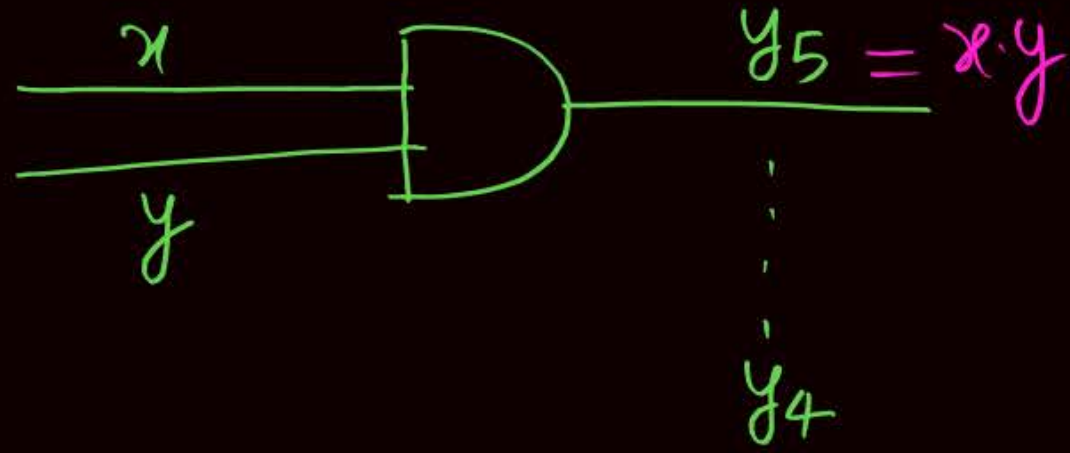

$y_0$



# [ Standard Combinational Circuits ]

- Half Adder ✓
- Half Subtractor ✓
- Full Adder ✓
- Full Subtractor ✓

$$\begin{array}{r} (786)_{10} \\ + (259)_{10} \end{array}$$

	7	8	6
	2	5	9
	1	1	
1	0	4	5

	3	6
	8	2
	0	
1	1	8

$$\begin{array}{r} \Rightarrow \begin{array}{c} 8^1 8^0 \\ (26)_8 \end{array} = (16+6)_{10} = (22)_{10} \\ + \begin{array}{c} (35)_8 \\ 1 \end{array} = (24+5)_{10} = (29)_{10} \end{array}$$

$$\begin{array}{r} (063)_8 \\ \hline \end{array} = (48+3)_{10} = (51)_{10}$$

$$\begin{array}{r} \begin{array}{c} 6^1 6^0 \\ (24)_6 \end{array} = (12+4)_{10} \\ + \begin{array}{c} (53)_6 \\ 1 \end{array} = (30+3)_{10} \\ \hline \begin{array}{c} 6^2 1 \\ (121)_6 \end{array} = (36+12+1)_{10} \end{array}$$



$$\begin{matrix} 8^1 & 8^0 \\ (3 & 6) \end{matrix}_8 = (24 + 6)_{10}$$

$$(4 \ 2)_8 = (32 + 2)_{10}$$

$$\begin{matrix} 8^2 & 8^1 & 8^0 \\ \hline (1 & 0 & 0) \end{matrix}_8 = (64 + 0 + 0)_{10}$$


$$\begin{matrix} \bullet & (3 \ 2)_8 \\ & (4 \ 5)_8 \\ & 0 \\ \hline & (0 \ 7 \ 7)_8 \end{matrix}$$

$$\begin{matrix} \bullet & (101)_2 \\ & + (101)_2 \\ \hline \end{matrix}$$

$$\begin{array}{cccc} 1 & 0 & 1 & \\ 1 & 0 & 1 & \\ \hline 1 & 0 & 1 & 0 \end{array}$$

Diagram illustrating the addition of two binary numbers (101)<sub>2</sub> + (101)<sub>2</sub>. The result is 1010<sub>2</sub>. The digits are grouped by color: the first '1' is blue, the '0' is pink, the second '1' is green, and the final '0' is blue.

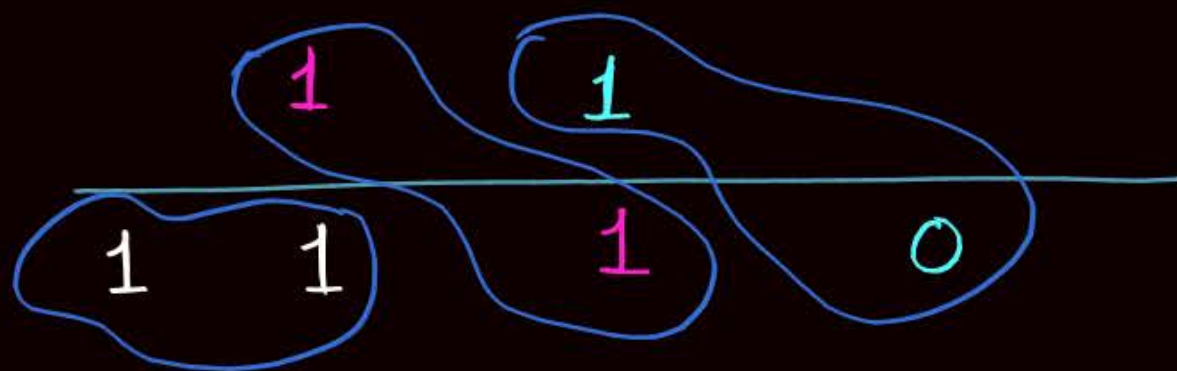
$$\begin{array}{r}
 (1\ 1\ 1)_2 \\
 + (1\ 1\ 1)_2
 \end{array}$$





$$A = a_3 \ a_2 \ a_1 \ a_0$$

$$B = + \ b_3 \ b_2 \ b_1 \ b_0$$

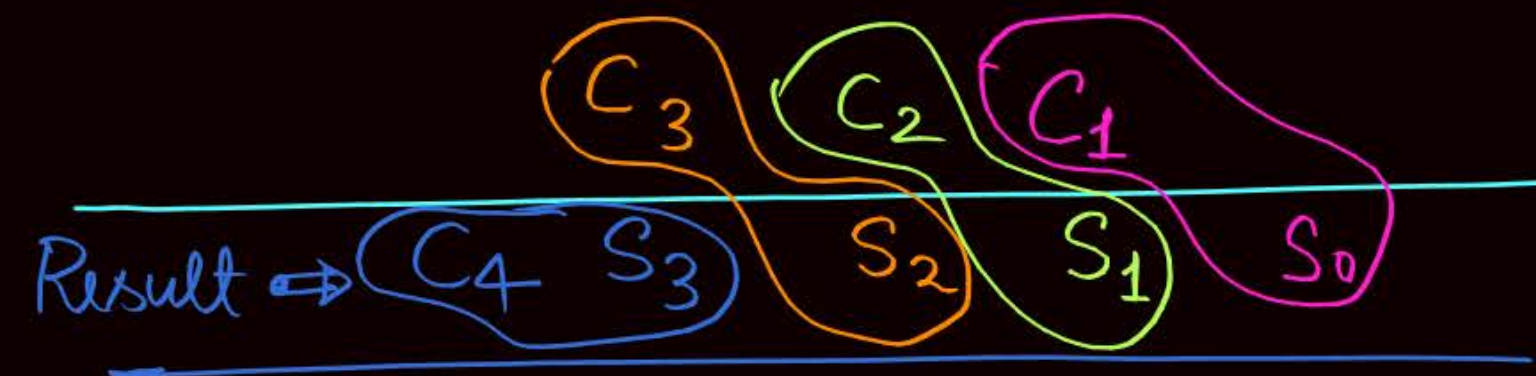



## 2 Minute Summary

→ Comb. CKt.



**Thank you**

**GW**  
*Soldiers !*

